



# Learn Git and GitHub without any code!

Using the Hello World guide, you'll start a branch, write comments, and open a pull request.

Read the guide

 [Zuzanaczm](#) / [Digital-electronics-1](#)

<> Code

! Issues

🔗 Pull requests

▶ Actions

📁 Projects

📖 Wiki

🛡️ Security

🔗 main ▾

[Digital-electronics-1](#) / [Labs](#) / [02-logic](#) /



Zuzanaczm Update readme.md ...

10 minutes ago  History

..



images

20 minutes ago



readme.md

10 minutes ago

readme.md



## Zuzana Czmelová - Lab assignment 2 (logic)

[GitHub repository - 02\\_logic](#)

### Part 1 - Truth table

Dec. equivalent

B[1:0]

A[1:0]

B > A

B = A

B < A

Dec. equivalent	B[1:0]	A[1:0]	B > A	B = A	B < A
0	0 0	0 0	0	1	0
1	0 0	0 1	0	0	1
2	0 0	1 0	0	0	1
3	0 0	1 1	0	0	1
4	0 1	0 0	1	0	0
5	0 1	0 1	0	1	0
6	0 1	1 0	0	0	1
7	0 1	1 1	0	0	1
8	1 0	0 0	1	0	0
9	1 0	0 1	1	0	0
10	1 0	1 0	0	1	0
11	1 0	1 1	0	0	1
12	1 1	0 0	1	0	0
13	1 1	0 1	1	0	0
14	1 1	1 0	1	0	0
15	1 1	1 1	0	1	0

## Part 2 - A 2-bit comparator

---

B = A


		A1 A0			
		00	01	11	10
B1 B0	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	1

$$B = A_{SoP}^{canon} = (\bar{a}_1 \cdot \bar{a}_0 \cdot \bar{b}_1 \cdot \bar{b}_0) + (\bar{a}_1 \cdot a_0 \cdot \bar{b}_1 \cdot b_0) + (a_1 \cdot \bar{a}_0 \cdot b_1 \cdot \bar{b}_0) + (a_1 \cdot a_0 \cdot b_1 \cdot b_0)$$

**B>A**

		A1 A0			
		00	01	11	10
B1 B0	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0
 
$$B > A_{SoP}^{min} = (\bar{a}_1 \cdot b_1) + (\bar{a}_1 \cdot \bar{a}_0 \cdot b_0) + (\bar{a}_0 \cdot b_1 \cdot b_0)$$



## Part 3 - A 4-bit comparator

Link to EDA playground of 4-bit comparator simulation

[My EDA Playground](#)

### Design

```
-- Entity declaration for 4-bit binary comparator

entity comparator_4bit is
    port(
        a_i      : in  std_logic_vector(4 - 1 downto 0);
        b_i      : in  std_logic_vector(4 - 1 downto 0);
        --
        B_greater_A_o  : out std_logic;
        B_equals_A_o   : out std_logic;
        B_less_A_o     : out std_logic
    );
end entity comparator_4bit;

-- Architecture body for 4-bit binary comparator

architecture Behavioral of comparator_4bit is
begin
```

```

B_greater_A_o  <= '1' when (b_i > a_i) else '0';
B_equals_A_o   <= '1' when (b_i = a_i) else '0';
B_less_A_o     <= '1' when (b_i < a_i) else '0';

```

```
end architecture Behavioral;
```

## Stimulus process from testbench file (testbench.vhd)

```

library ieee;
use ieee.std_logic_1164.all;

-- Entity declaration for testbench

entity tb_comparator_4bit is

end entity tb_comparator_4bit;

-- Architecture for testbench

architecture testbench of tb_comparator_4bit is

    -- Local signals
    signal s_a      : std_logic_vector(4 - 1 downto 0);
    signal s_b      : std_logic_vector(4 - 1 downto 0);
    signal s_B_greater_A : std_logic;
    signal s_B_equals_A  : std_logic;
    signal s_B_less_A    : std_logic;

begin
    -- Connecting testbench signals with comparator_2bit entity (Unit Under Te
    uut_comparator_4bit : entity work.comparator_4bit
        port map(
            a_i      => s_a,
            b_i      => s_b,
            B_greater_A_o => s_B_greater_A,
            B_equals_A_o  => s_B_equals_A,
            B_less_A_o    => s_B_less_A
        );

    -----
    -- Data generation process
    -----

    p_stimulus : process
    begin
        -- Report a note at the begining of stimulus process
        report "Stimulus process started" severity note;

```

```
-- 1st test value
s_b <= "0000"; s_a <= "0000"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0000" severity error;

-- 2nd test value
s_b <= "0000"; s_a <= "0001"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0001" severity error;

-- 3rd test value
s_b <= "0000"; s_a <= "0010"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0010" severity error;

-- 4th test value
s_b <= "0000"; s_a <= "0011"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0000, 0011" severity error;

-- 5th test value
s_b <= "0001"; s_a <= "0000"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0001, 0000" severity error;

-- 6th test value
s_b <= "0001"; s_a <= "0001"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0001, 0001" severity error;

-- 7th test value
s_b <= "0001"; s_a <= "0010"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0001, 0010" severity error;

-- 8th test value
s_b <= "0001"; s_a <= "0011"; wait for 100 ns;
```

```

-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0001, 0011" severity error;

-- 9th test value
s_b <= "0010"; s_a <= "0000"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0010, 0000" severity error;

-- 10th test value
s_b <= "0010"; s_a <= "0001"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0010, 0001" severity error;

-- Error test value
s_b <= "0011"; s_a <= "0011"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0011, 0011" severity error;

-- 11th test values
s_b <= "0100"; s_a <= "0000"; wait for 100 ns;
-- Expected output
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A
-- If false, then report an error
report "Test failed for input combination: 0100, 0000" severity error;

-- Report a note at the end of stimulus process
report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

end architecture testbench;

```

## Console output

```
[2021-02-22 07:46:28 EST] ghdl -i design.vhd testbench.vhd && ghdl -m tb_comparator_4bit && ghdl -r tb_comparator_4bit --vcd=dump.vcd && sed -i 's/\0/X/g; s/\1-/X/g; s/\0/1/g;
analyze design.vhd
analyze testbench.vhd
elaborate tb_comparator_4bit
testbench.vhd:40:9:00ms:(report note): Stimulus process started
testbench.vhd:118:9:01100ns:(assertion error): Test failed for input combination: 0011, 0011
testbench.vhd:132:9:01200ns:(report note): Stimulus process finished
Finding VCD file...
./dump.vcd
[2021-02-22 07:46:30 EST] Opening EPWave...
Done
```

## Simulated waveforms

