



Learn Git and GitHub without any code!

Using the Hello World guide, you'll start a branch, write comments, and open a pull request.

Read the guide

 Zuzanaczm / Digital-electronics-1

<> Code

! Issues

🔗 Pull requests

▶ Actions

📁 Projects

📖 Wiki

🛡️ Security

🔗 main ▾



Digital-electronics-1 / Labs / 05-counter / readme.md



Zuzanaczm Update readme.md

🕒 History

👤 1 contributor

Raw

Blame



167 lines (127 sloc) | 4.04 KB

Lab assignment - Zuzana Czmelová (binary counter)

Part 1 - Pin connections & table

Time interval	Number of clk	Number of clk periods	Number of clk periods in binary
---------------	---------------	-----------------------	---------------------------------

	periods	in hex	
2 ms	200 000	x"3_0d40"	b"0011_0000_1101_0100_0000"
4 ms	400 000	x"6_1A80"	b"0110_0001_1010_1000_0000"
10 ms	1 000 000	x"F_4240"	b"1111_0100_0010_0100_0000"
250 ms	25 000 000	x"17D_7840"	b"0001_0111_1101_0111_1000_0100_0000"
500 ms	50 000 000	x"2FA_F080"	b"0010_1111_1010_1111_0000_1000_0000"
1 sec	100 000 000	x"5F5_E100"	b"0101_1111_0101_1110_0001_0000_0000"

Pin connections:

```

BTNL => P17
BTNR => M17
BTNU => M18
BTND => P18
BTNC => N17

```

Connections are active-high.

Part 2 - Bidirectional counter

A) VHDL code of the process p_cnt_up_down

```

p_cnt_up_down : process(clk)
begin
    if rising_edge(clk) then

        if (reset = '1') then                -- Synchronous reset
            s_cnt_local <= (others => '0'); -- Clear all bits

        elsif (en_i = '1') then              -- Test if counter is enabled

            if (cnt_up_i = '1') then
                s_cnt_local <= s_cnt_local + 1;
            else
                s_cnt_local <= s_cnt_local - 1;
            end if;
        end if;
    end if;
end process;

```

```

        end if;

    end if;
end process p_cnt_up_down;

```

B) VHDL reset and stimulus processes from testbench file tb_cnt_up_down.vhd

```

p_reset_gen : process
begin
    s_reset <= '1';
    wait for 50 ns;

    s_reset <= '0'; -- Reset deactivated
    wait for 185 ns;

    s_reset <= '1';
    wait for 50 ns;

    s_reset <= '0';
    wait for 200 ns;

    s_reset <= '1';
    wait for 20 ns;

    s_reset <= '0';
    wait;
end process p_reset_gen;

-----
-- Data generation process
-----

p_stimulus : process
begin
    report "Stimulus process started" severity note;

    -- Enable counting
    s_en      <= '1';

    -- Change counter direction
    s_cnt_up <= '1';
    wait for 380 ns;

    s_cnt_up <= '0';
    wait for 220 ns;

    s_cnt_up <= '1';
    wait for 220 ns;

```

```


s_cnt_up <= '0';
wait for 380 ns;

-- Disable counting
s_en      <= '0';

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

C) Screenshot of simulation

 

Part 3 - VHDL code from source file top.vhd

A) VHDL code

```

-----
-- Instance (copy) of clock_enable entity
clk_en0 : entity work.clock_enable
    generic map(
        g_MAX => 100000000
    )
    port map(
        clk    => CLK100MHZ,
        reset  => BTNC,
        ce_o   => s_en
    );

-----
-- Instance (copy) of cnt_up_down entity
bin_cnt0 : entity work.cnt_up_down

```

```

    generic map(
        g_CNT_WIDTH => 4
    )
    port map(
        clk      => CLK100MHZ,
        reset    => BTNC,
        en_i      => s_en,
        cnt_up_i  => SW(0),
        cnt_o     => s_cnt
    );

-- Display input value on LEDs
LED(3 downto 0) <= s_cnt;


-----

-- Instance (copy) of hex_7seg entity
hex2seg : entity work.hex_7seg
    port map(
        hex_i      => s_cnt,
        seg_o(6)   => CA,
        seg_o(5)   => CB,
        seg_o(4)   => CC,
        seg_o(3)   => CD,
        seg_o(2)   => CE,
        seg_o(1)   => CF,
        seg_o(0)   => CG
    );

```

B) Images of the top layer including both counters

4-bit bidirectional counter

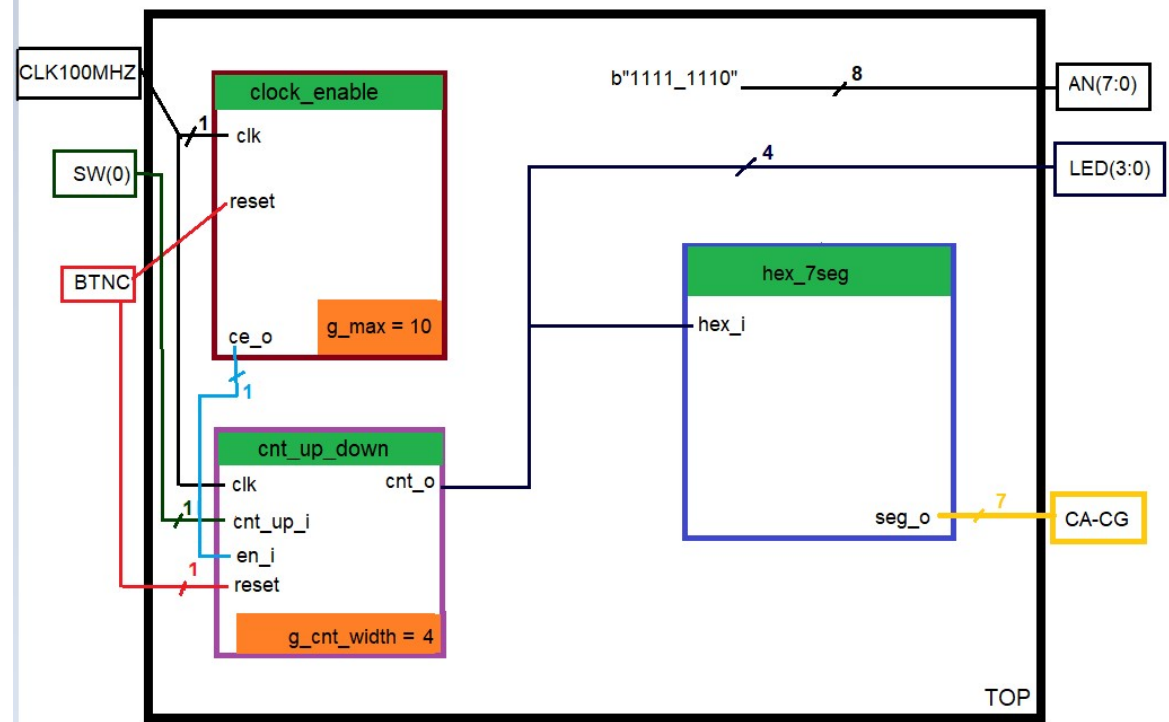

16-bit bidirectional counter

